

Sequential logic-2

EEE 241: Digital Logic Design

Department of Electrical and Computer Engineering

Lecture Contents

- Review
- Flip Flops
- SR Flip Flop
- D Flip Flop
- Jk Flip Flop
- T Flip Flop

Reference Readings and Acknowledgements

- Chapter 5: Digital Design with Introduction to Verilog HDL M. Morris Mano, Michael D. Ciletti, 5th Edition

Flip-Flops

- A trigger
 - The state of a latch or flip-flop is switched by a change of the control input
- Level triggered – latches
- Edge triggered – flip-flops



(a) Response to positive level




(b) Positive-edge response



(c) Negative-edge response

Fig. 5.8

Clock response in latch and flip-flop

 

- If level-triggered flip-flops are used
 - the feedback path may cause instability problem
- Edge-triggered flip-flops
 - the state transition happens only at the edge
 - eliminate the multiple-transition problem

Edge-triggered D flip-flop

- Master-slave D flip-flop
 - two separate flip-flops
 - a master flip-flop (positive-level triggered)
 - a slave flip-flop (negative-level triggered)


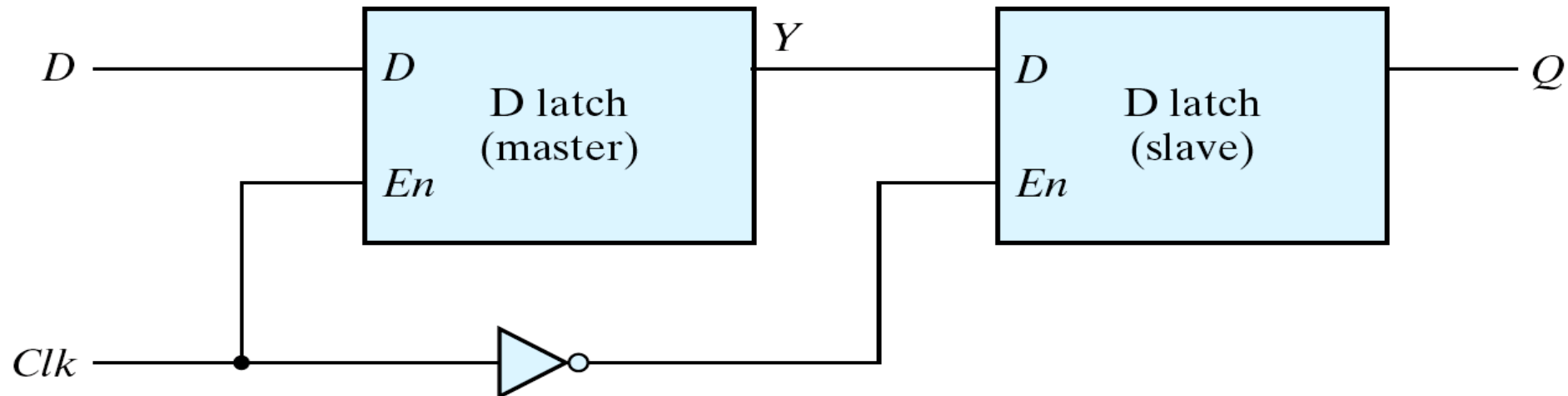
 


Fig. 5.9
Master-slave D flip-flop

 

- $CP = 1: (S,R) \Rightarrow (Y,Y')$; (Q,Q') holds
- $CP = 0: (Y,Y')$ holds; $(Y,Y') \Rightarrow (Q,Q')$
- (S,R) could not affect (Q,Q') directly
- the state changes coincide with the negative-edge transition of CP

- Edge-triggered flip-flops
 - the state changes during a clock-pulse transition
- A D-type positive-edge-triggered flip-flop

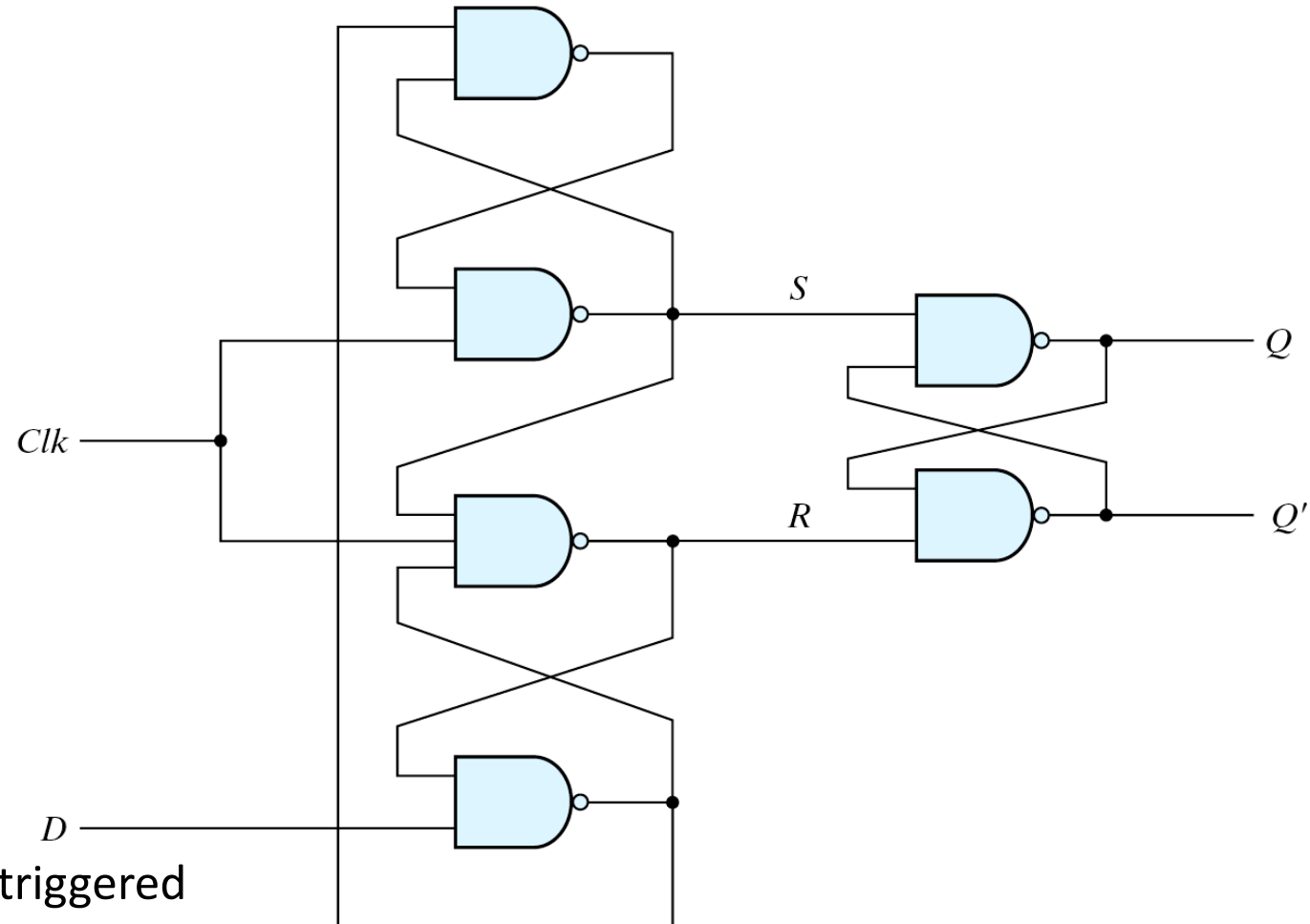


Fig. 5.10
D-type positive-edge-triggered
flip-flop

- three basic flip-flops
- $(S,R) = (0,1)$: $Q = 1$
- $(S,R) = (1,0)$: $Q = 0$
- $(S,R) = (1,1)$: no operation
- $(S,R) = (0,0)$: should be avoided



 


Fig. 5.10
D-type positive-edge-triggered
flip-flop

 


(a) With $CP = 0$

 

 (b) With $CP = 1$

- The setup time
 - D input must be maintained at a constant value prior to the application of the positive CP pulse
- The hold time
 - D input must not changes after the application of the positive CP pulse



- The propagation delay time
 - The interval between the trigger edge and the stabilization of the output to a new state


 


Fig. 10-4 Measurement of Propagation Delay


- Summary
 - $CP=0$: $(S,R) = (1,1)$, no state change
 - $CP=\uparrow$: state change once
 - $CP=1$: state holds

Other Flip-Flops

 - The edge-triggered D flip-flops
 - The most economical and efficient
 - Positive-edge and negative-edge



(a) Positive-edge

 


(a) Negative-edge


Fig. 5.11
Graphic symbols for edge-triggered *D* flip-flop

Fig. 5.12 JK flip-flop

 - JK flip-flop
 - $D = JQ' + K'Q$
 - J=0, K=0: D=Q, no change
 - J=0, K=1: D=0, Q=0
 - J=1, K=0: D=1, Q=1
 - J=1, K=1: D=Q', Q=Q'



(a) Circuit diagram

 



(b) Graphic symbol

Fig. 5.13


T flip-flop

- T flip-flop

  
- $D = T \oplus Q = TQ' + T'Q$
 - T=0: D=Q, no change
 - T=1: D=Q' , Q=Q'



(c) Graphic symbol

 

(a) From JK flip-flop

 

(b) From D flip-flop

- Characteristic tables

Table 5.1
Flip-Flop Characteristic Tables

JK Flip-Flop

<i>J</i>	<i>K</i>	<i>Q(t + 1)</i>	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

D Flip-Flop

<i>D</i>	<i>Q(t + 1)</i>	
0	0	Reset
1	1	Set



T Flip-Flop

<i>T</i>	<i>Q(t + 1)</i>	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

- Characteristic equations
 - D flip-flop
 - $Q(t+1) = D$
 - JK flip-flop
 - $Q(t+1) = JQ' + K'Q$
 - T flop-flop
 - $Q(t+1) = T \oplus Q$

Direct inputs

 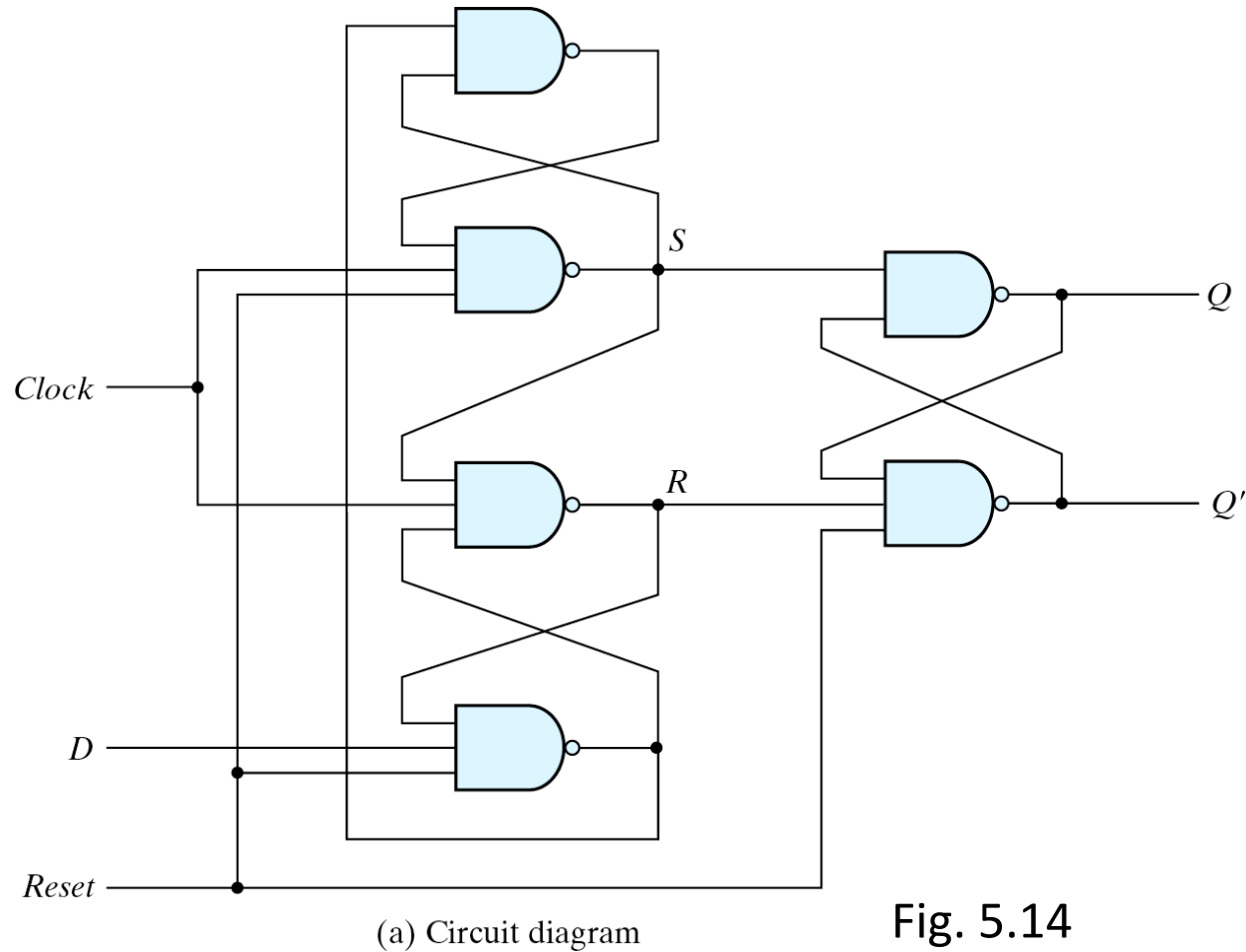- asynchronous set and/or asynchronous reset



R	Clk	D	Q	Q'
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

(b) Function table

Fig. 5.14

D flip-flop with asynchronous reset